
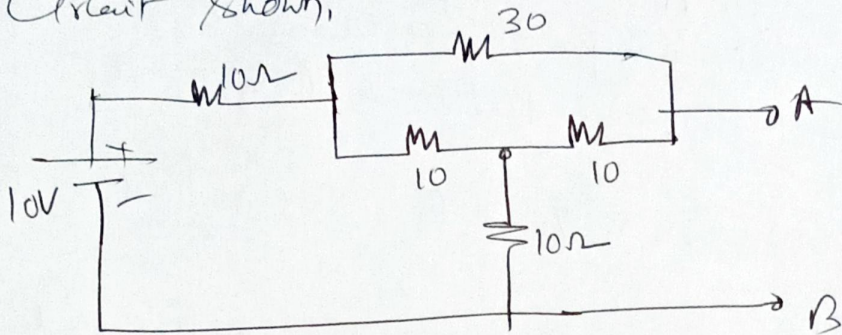

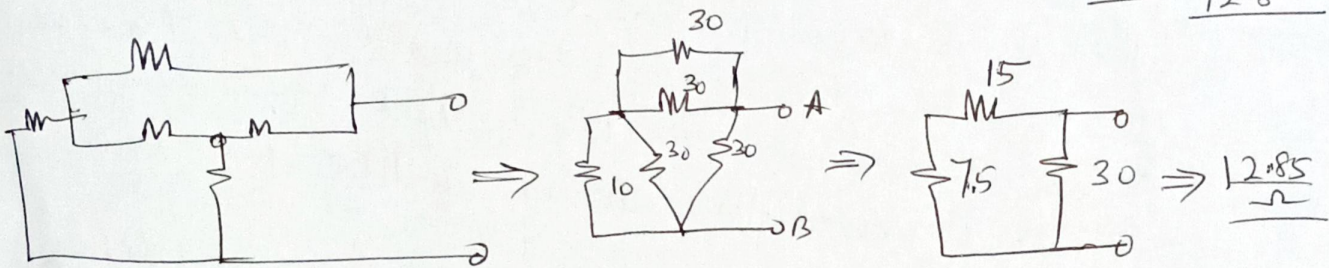
### Problem 3.


Find Thevenin Equivalent Circuit across AB of the Circuit shown,



Ans:  $\frac{4.28V}{12.8\Omega}$





TV for  $V_{th}$

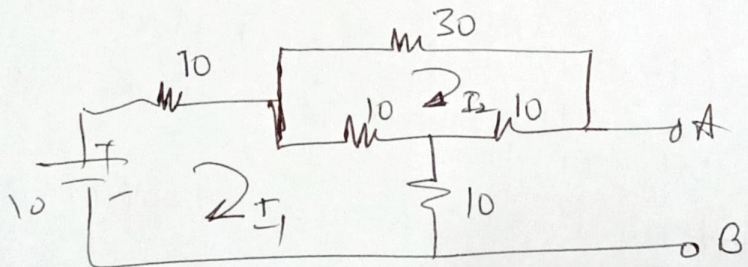

By Matrix Method  $\begin{bmatrix} 30 & -10 \\ -10 & 50 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 10 \\ 0 \end{bmatrix}$

$I_1 = 0.35A, I_2 = 0.071A$

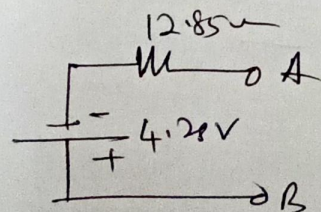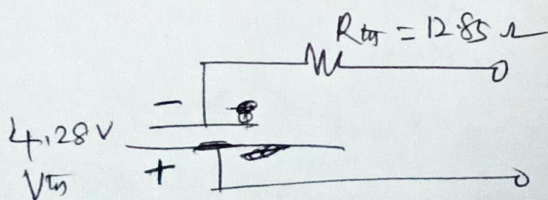$V_{th} = (-10 \times 0.071) - (10 \times 0.35) = -4.28V$





## 5. Maximum Power Transfer Theorem:- (MPTT)

- In many applications of the circuits, requires the maximum power available from a source to be transferred to Load Resistor  $R_L$ .
- Maximum of 50% of the power can be transferred to  $R_L$ .
- Consider a signal received at the antenna of FM-Radio Receiver from a distant station. The Receiver Circuit is designed so that Maximum power is available at the output of amplifier circuit connected to antenna of the FM-Radio.
- Thus we represent FM antenna and amplifier by Thevenin's Equivalent Circuit.

Statement:- The Maximum Power transfer theorem states that the, maximum power delivered by a source represented by its Thevenin's Equivalent Circuit is attained by Load Resistance  $R_L$  equal to Thevenin's Resistance  $R_{th}$ .


### Steps to be followed

- The given circuit represented in Thevenin's Equivalent Circuit
- Equate Thevenin's Resistance = Load Resistance  $R_L$
- Calculate Maximum power using the formula  $P_{max} = I_L^2 R_L$  where  $I_L$  is Load current.



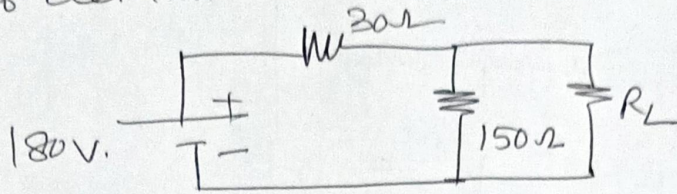
Problem 1

Find the Load  $R_L$  will result in maximum power deliver to Load for the circuit shown. Also determine the Maximum Power.




Ans:  $25\Omega$   
225Watt

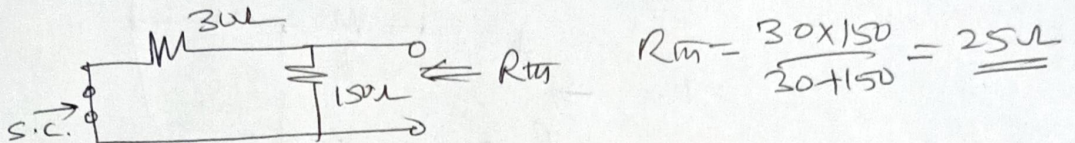Solution:- First find Thevenin's resistance  $R_{th}$ .




Find open circuit voltage between A & B.

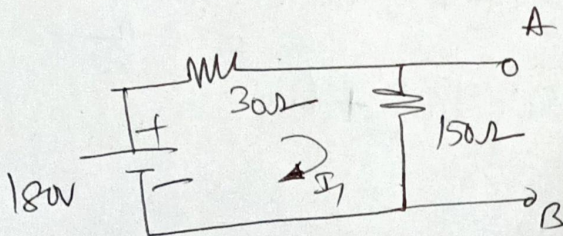

$$I_1 = \frac{180}{180} = 1A$$

$$\therefore V_{AB} = 150 \times 1 = \underline{\underline{150V}} \\ = V_{th}$$

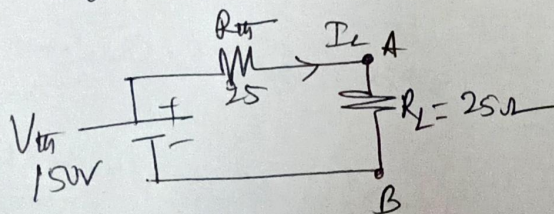Represent the given circuit in Thevenin's circuit.  
and Equate  $R_L = R_{th} = 25\Omega$




$$I_L = \frac{150}{25 + 25} = \underline{\underline{3A}}$$

$$\therefore P_{max} = I_L^2 R_L = 3^2 \times 25 = \underline{\underline{225 \text{ Watts}}}$$

$$\underline{\underline{OR}} \quad \underline{\underline{P_{max}}} = \frac{V_{th}^2}{4R_L} = \frac{150 \times 150}{4 \times 25} = \underline{\underline{225 \text{ Watts}}}$$



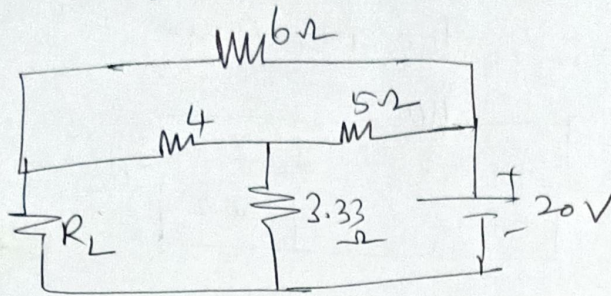
Problem: 2 Find the value of  $R_L$  for Maximum Power (10)  
~~transfer~~ transfer to it. Find the value of max Power



Ans: 3Ω  
16.32 Watts


Solution

To find  $R_{th}$

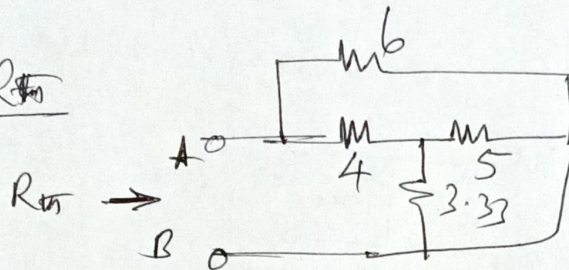

$$R_{th} = \frac{\left\{ \frac{(5 \times 3.33)}{(5 + 3.33)} + 4 \right\} \times 6}{\left\{ \frac{(5 \times 3.33)}{(5 + 3.33)} + 4 \right\} + 6} = \underline{\underline{3\Omega}}$$

By Mesh Equations

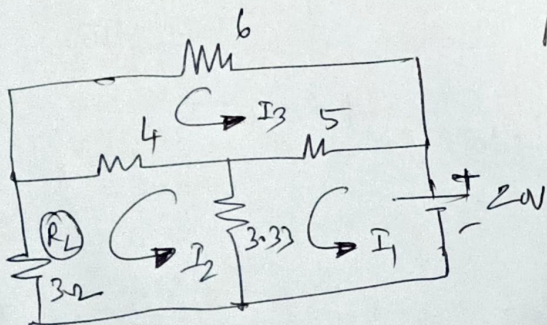


$$\begin{bmatrix} 8.33 & -3.33 & -5 \\ -3.33 & 10.33 & -4 \\ -5 & -4 & 15 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} +20 \\ 0 \\ 0 \end{bmatrix}$$

$\frac{I_2}{2} = 2.33A$  is the Load Current

$$\therefore P_{max} = I_L^2 R_L = 2.33^2 \times 3 = \underline{\underline{16.328W}}$$



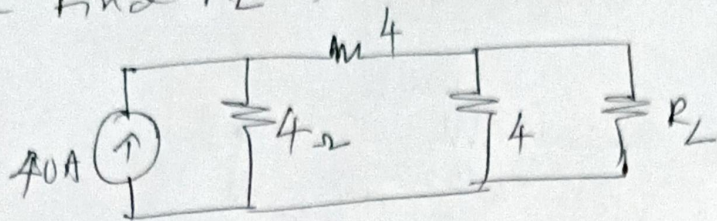Problem 3:- Find  $R_L$  and Maximum Power Transferred to  $R_L$  (11)




ANSWER


$$R_{th} = 2.67\Omega$$

$$P_{max} = 267W$$

Solution:-

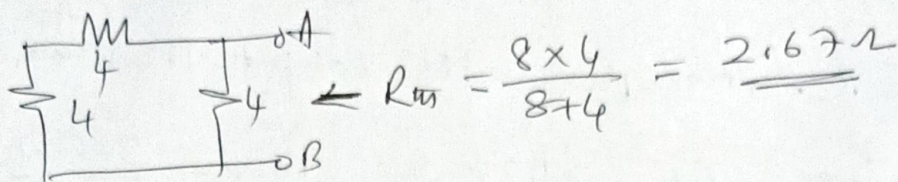

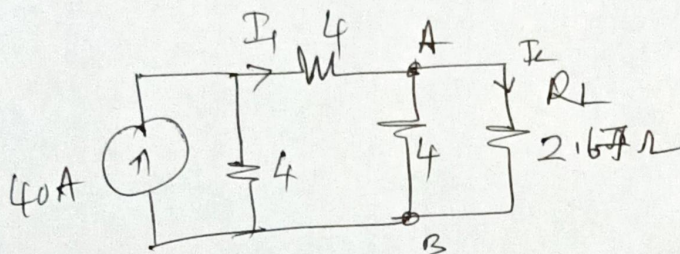Use the formula  $\left. \begin{matrix} \text{Branch} \\ \text{Current} \end{matrix} \right\} = \frac{\text{Main Current} \times \text{Resistance of other Branch}}{\text{Sum of Resistances}}$



$$I_1 = \frac{40 \times 4}{4 + [4 + (4 || 2.67)]} = 16.66A$$

$$I_L = \frac{16.66 \times 4}{4 + 2.67} = 10A$$


$$P_{max} = I_L^2 R_L = 10^2 \times 2.67 = 267W$$



Problem no 4

Home work

(12)

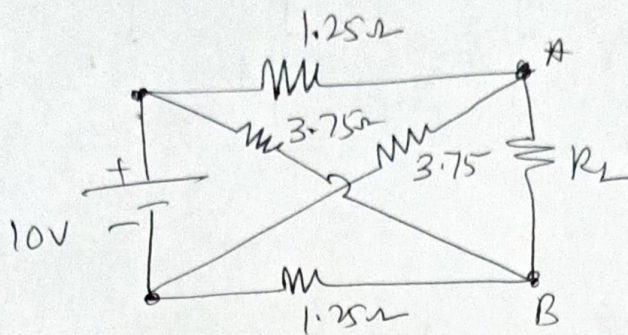

Find  $R_L$  for Max Power. Also compute the value of Max Power.

Ans:-  $R_{th} = \underline{\underline{1.875\Omega}}$ ,  $P_{max} = \underline{\underline{3.33W}}$