

## Superposition Theorem


(1)

- When Current source & Voltage source both are present

- Consider voltage source alone and open circuit current source. Then find load current.
- Consider current source alone and short circuit voltage source, find the load current.

By Superposition theorem Add both the currents if it is in same direction.

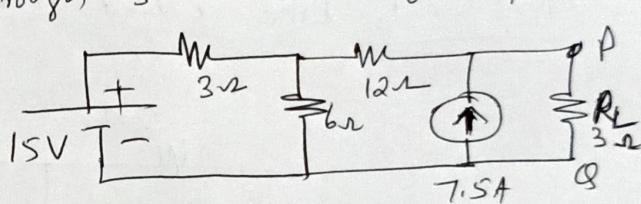Example :- Find current through  $3\Omega$  Resistor By Superposition Theorem




When 15V acting alone, Open circuit 7.5A source

$$\begin{bmatrix} 9 & -6 \\ -6 & 21 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 15 \\ 0 \end{bmatrix}$$

$\therefore I_2 = 0.588 \text{ A}$  from P to Q

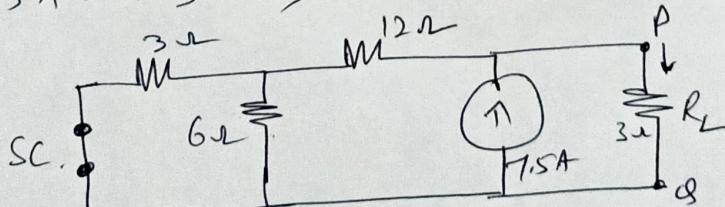When 7.5A acting alone, Short circuit 15V Battery, Draw the circuit



Using Current Division formula  $I_{PQ} = \frac{7.5 \times \left[ \frac{3 \times 6}{3+6} + 12 \right]}{\frac{3 \times 6}{3+6} + 12 + 3} = 6.17 \text{ A}$


$\therefore 6.17 \text{ A}$  from P to Q

By Superposition theorem } = 0.588 + 6.17 =  $\frac{6.7647 \text{ Amp}}{\text{ANSWER}}$

Current thru  $R_L$


Home Work Using Superposition Theorem find (2)

Current thro'  $2\Omega$  resistor.

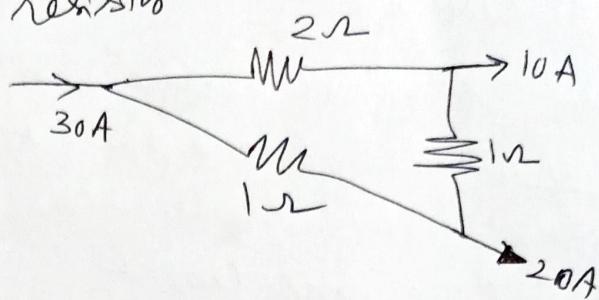

ANSWER: 10 Amps.

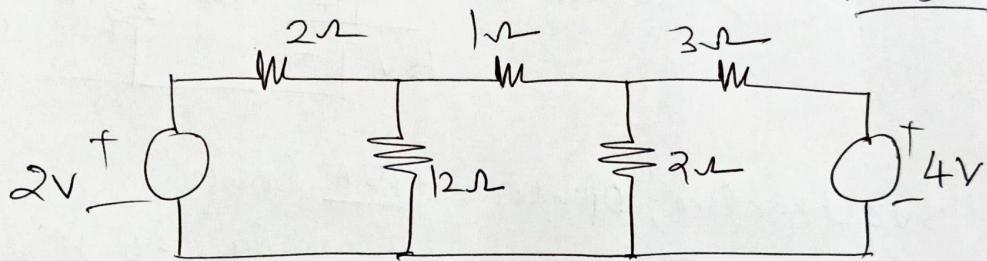Home Work: Find current thro'  $3\Omega$  resistor by Superposition Theorem



ANSWER :-


$$0.1752 - 0.9635$$

$$= \underline{\underline{0.7883A}} \text{ ANSWER}$$
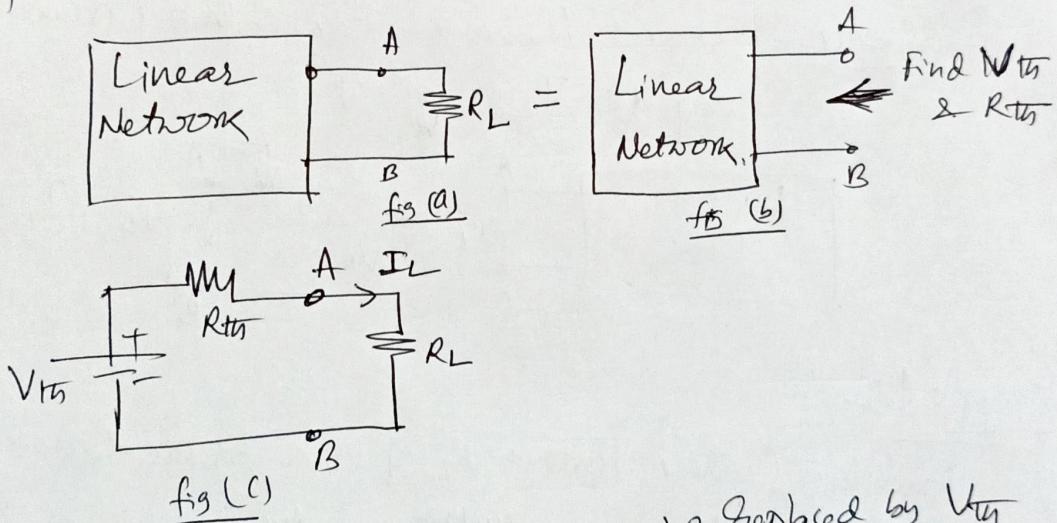
#### (A): Thevenin's theorem:-

- This theorem is very ~~helpful~~ helpful in finding current through voltage across of any complicated network consisting of more number of sources and resistors.

Statement:-  
Any Linear network consisting of emf's and resistors can be replaced by an equivalent voltage source  $V_{th}$  in series with an resistor  $R_{th}$ , when seen from two points A & B as shown in the figure (b)



- As shown in fig(c), the entire circuit is replaced by  $V_{th}$  and  $R_{th}$  as shown. Connect  $R_L$  between A & B. Then find load current.  $\therefore I_L = \frac{V_{th}}{R_{th} + R_L}$


Where  $V_{th}$  is called open circuit voltage or Thevenin's voltage and is calculated from circuit b.  
 $R_{th}$  is called open circuit resistance or Thevenin's resistor and is calculated from circuit b

(4)

## Steps involved in solution of Network using

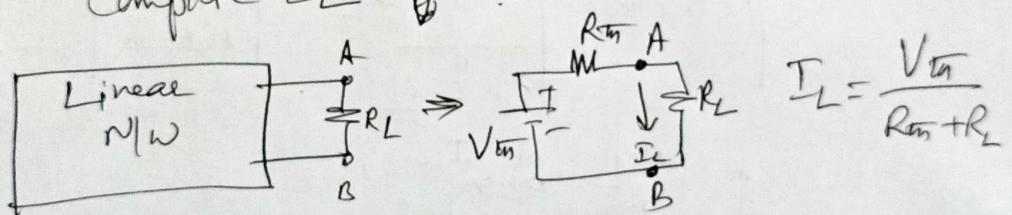
### Thevenin's Theorem

- Step 1:- Remove the Load Resistance and mark as A & B
- Step 2:- To find  $R_{th}$ , replace all Voltage sources by their internal resistance and Current source by open circuit  
Find Resistance Across A & B, this gives  $R_{th}$ .
- Step 3:- find the open circuit voltage  $V_{AB}$  for the Step 1 Circuit, and is called  $V_{th}$ .
- Step 4:- Draw Thevenin's Equivalent Circuit, Then Compute  $I_L$   $\&$   $\$$



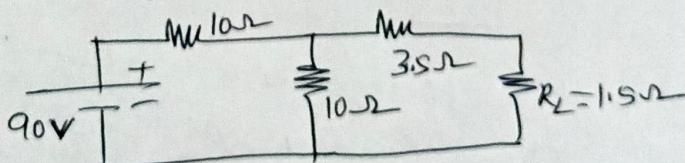
### Example 1:-

Find the current through  $R_L$  of  $1.5\Omega$ , for the circuit shown in the figure.




Answer: 4.5A

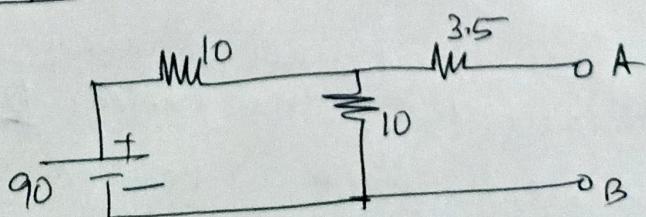Solution:- I-step — Remove  $R_L$  and Mark A and B



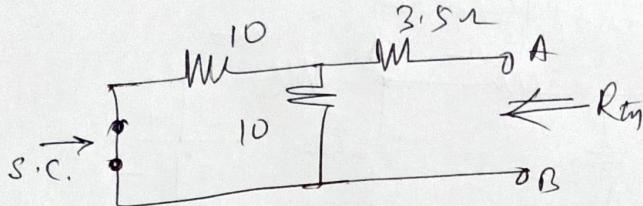
(5)

**II-step** — To find  $R_{th}$ , replace All Voltage source by short circuit



$$\therefore R_{th} = \frac{(10 \times 10)}{(10 + 10)} + 3.5 = \underline{\underline{8.5 \Omega}} = R_{th}.$$

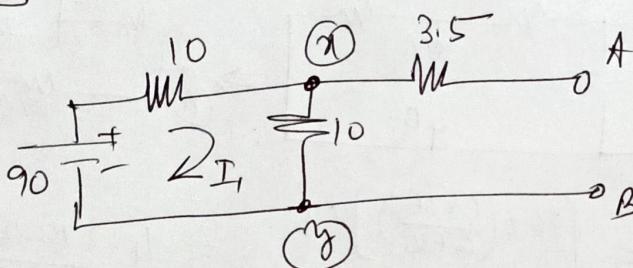**III-step** — To find  $V_{Th}$ , find open circuit voltage of  $\frac{\text{Step-1 Circuit}}$




— Here the voltage across AB is equal to voltage across 10Ω  
∴  $V_{AB} = V_{Th}$

— Let  $I_1$  be the mesh current ∴  $I_1 = \frac{90}{10+10} = \underline{\underline{4.5A}}$

— ∵  $V_{AB} = 10 \times 4.5 = 45V = V_{Th}$

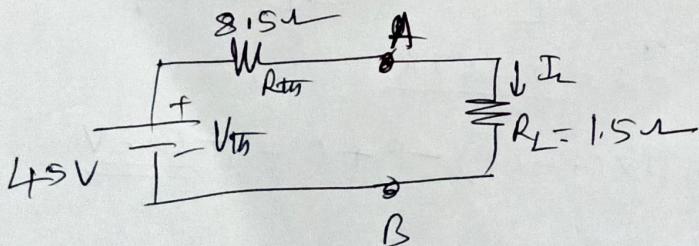**IV step** Write Thevenin's Equivalent Circuit then find  $I_L$




$$I_L = \frac{V_{th}}{R_{th} + R_L} = \frac{45}{8.5 + 1.5} = \underline{\underline{4.5A}} \quad \underline{\underline{\text{Answer}}}$$

(6)


**Problem 2**

Find current through 6Ω resistor using


Thevenin's Theorem

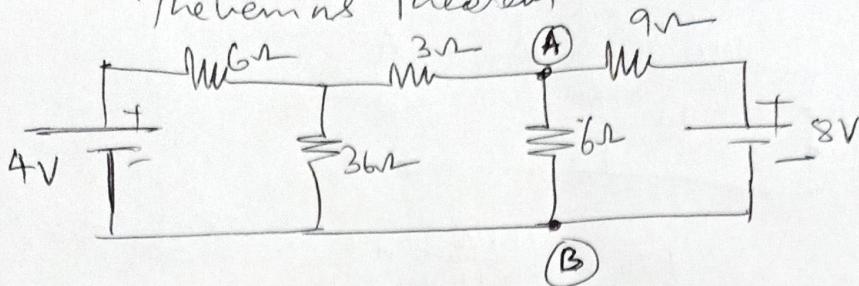

$$\underline{\underline{\text{Ans: } 0.545 \text{ A}}}$$

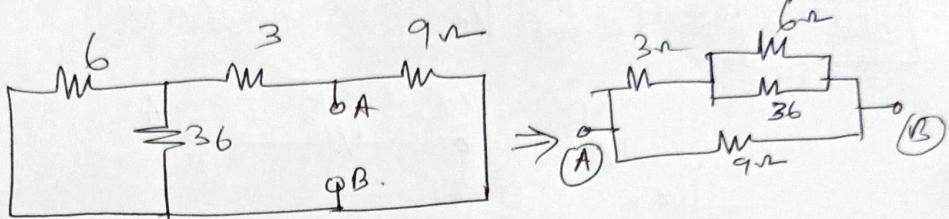**Solution**To find  $R_{th}$ 

$$R_{AB} = R_{th} = \frac{[3 + \left(\frac{6 \times 36}{6+36}\right)] \times 9}{3 + \left(\frac{6 \times 36}{6+36}\right) + 9} = \underline{\underline{4.275 \Omega}}$$

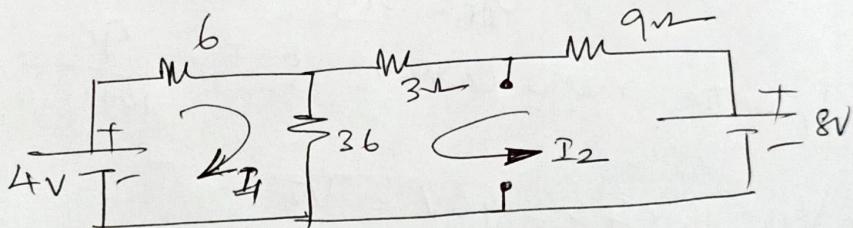
To find  $V_{th}$ 

By Matrix Method

$$\begin{bmatrix} 42 & +36 \\ +36 & 48 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} +4 \\ +8 \end{bmatrix}$$

$$\underline{\underline{I_2 = 0.2667 \text{ A}}}$$

$$\therefore V_{th} = (9 \times 0.2667) - 8 + 0 = \underline{\underline{-5.6 \text{ V}}}$$

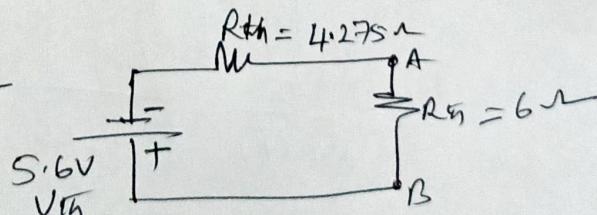
Thevenin Equivalent

$$I_L = \frac{5.6}{4.275 + 6} = \underline{\underline{0.545 \text{ A}}}$$

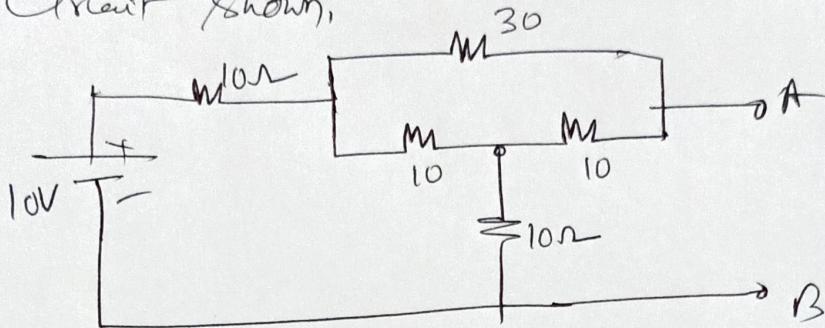
Problem 3.

7


Find Thevenin Equivalent Circuit across  $\underline{AB}$  of the Circuit shown,


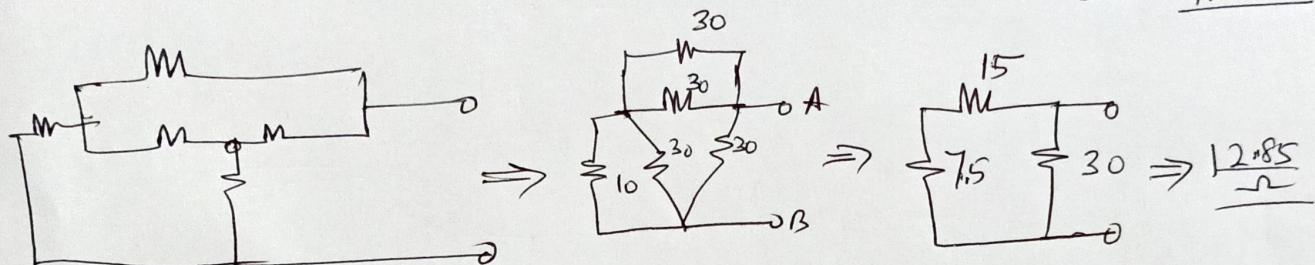
$$\text{Ans: } \frac{4.28V}{12.8\Omega}$$



To find  $V_{th}$

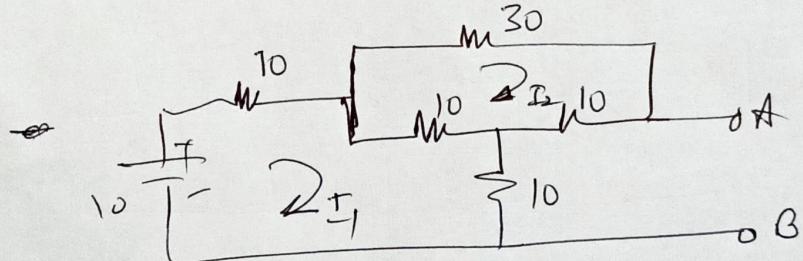

By Matrix Method

$$\begin{bmatrix} 30 & -10 \\ -10 & 50 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 10 \\ 0 \end{bmatrix}$$

$$I_1 = 0.35A, \quad I_2 = 0.071A$$

$$V_{th} = (10 \times 0.071) - (10 \times 0.35) = -4.28V$$

